

Unit5

- Performing operations at different rates
- Using separate state machines running in parallel
 - Find the GCD of different rates
 - e.g. one blinks at 2 Hz, another at 5 Hz, then should stay on/off for 250/100ms, GCD = 50 ms

Unit6

- Step 1: Define a mask that has 1's where the bits are to be copied
 - #define MASKBITS 0xf0
- Step 2: Clear those bits in the destination register using the MASK
 - PORTB &= ~MASKBITS
- Step 3: Shift the bits of x to align them appropriately, then perform the regular step 3
 - PORTB |= ((x<<4) & MASKBITS);

Unit7

Applying Minterms to Synthesize a Function

- Each numbered **minterm** checks whether the inputs are equal to the corresponding combination. When the inputs are equal, the **minterm** will evaluate to 1 and thus the whole function will evaluate to 1.

x	y	z	P
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

use...

$$P = m_2 + m_3 + m_5 + m_7$$

$$= x'yz' + x'yz + xy'z + xyz$$

when $x,y,z = \{0,1,0\} = 2$ then

$$P = 0' \cdot 1 \cdot 0' + 0' \cdot 1 \cdot 0 + 0 \cdot 1' \cdot 0 + 0 \cdot 1 \cdot 0$$

$$= 1 + 0 + 0 + 0 = 1$$

when $x,y,z = \{1,0,1\} = 5$ then

$$P = 1' \cdot 0 \cdot 1' + 1' \cdot 0 \cdot 1 + 1 \cdot 0' \cdot 1 + 1 \cdot 0 \cdot 1$$

$$= 0 + 0 + 1 + 0 = 1$$

when $x,y,z = \{0,0,1\} = 1$ then

$$P = 0' \cdot 0 \cdot 1' + 0' \cdot 0 \cdot 1 + 0 \cdot 0' \cdot 1 + 0 \cdot 0 \cdot 1$$

$$= 0 + 0 + 0 + 0 = 0$$

Applying Maxterms to Synthesize a Function

- Each output that should produce a '0' can be checked-for with an OR gate
 - We refer to that OR-gate checker as a Maxterm of the function (M_i) where i represents the decimal value of the binary combination being checked
- We then AND together the maxterms

x	y	z	P	use...
0	0	0	0	M_0
0	0	1	0	M_1
0	1	0	1	
0	1	1	1	
1	0	0	0	M_4
1	0	1	1	
1	1	0	0	M_6
1	1	1	1	

$$P = M_0 \cdot M_1 \cdot M_4 \cdot M_6$$

$$= (x+y+z) \cdot (x+y+z') \cdot (x'+y+z) \cdot (x'+y'+z)$$

when $x,y,z = \{0,0,1\} = 1$ then

$$P = (0+0+1) \cdot (0+0+1') \cdot (0'+0+1) \cdot (0'+0'+1)$$

$$= 1 \cdot 0 \cdot 1 \cdot 1 = 0$$

when $x,y,z = \{1,1,0\} = 6$ then

$$P = (1+1+0) \cdot (1+1+0') \cdot (1'+1+0) \cdot (1'+1'+0)$$

$$= 1 \cdot 1 \cdot 1 \cdot 0 = 0$$

when $x,y,z = \{1,1,1\} = 7$ then

$$P = (1+1+1) \cdot (1+1+1') \cdot (1'+1+1) \cdot (1'+1'+1)$$

$$= 1 \cdot 1 \cdot 1 \cdot 1 = 1$$


- Using Boolean algebra theorems to simplify
- Applying DeMorgan's theorem and its gate equivalents

Unit8

- K-Maps (up to 4 variables, Don't cares, etc.)
- Implementing an arbitrary combinational function by converting a word description to a truth table and then implementing the circuit using K-Maps

Unit9

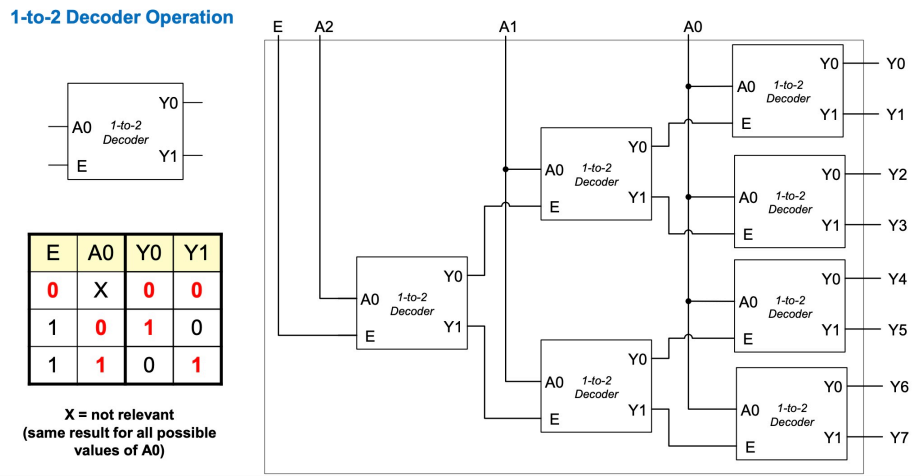- Build a 3-to-8 decoder from 1-to-2 decoders



- Full decoders and their implementation
- Enables and decoders
- Mux operation
- Designing muxes at the gate level
- Designing muxes from smaller muxes

Unit10

- Interrupts